

# Lab 1: pin out

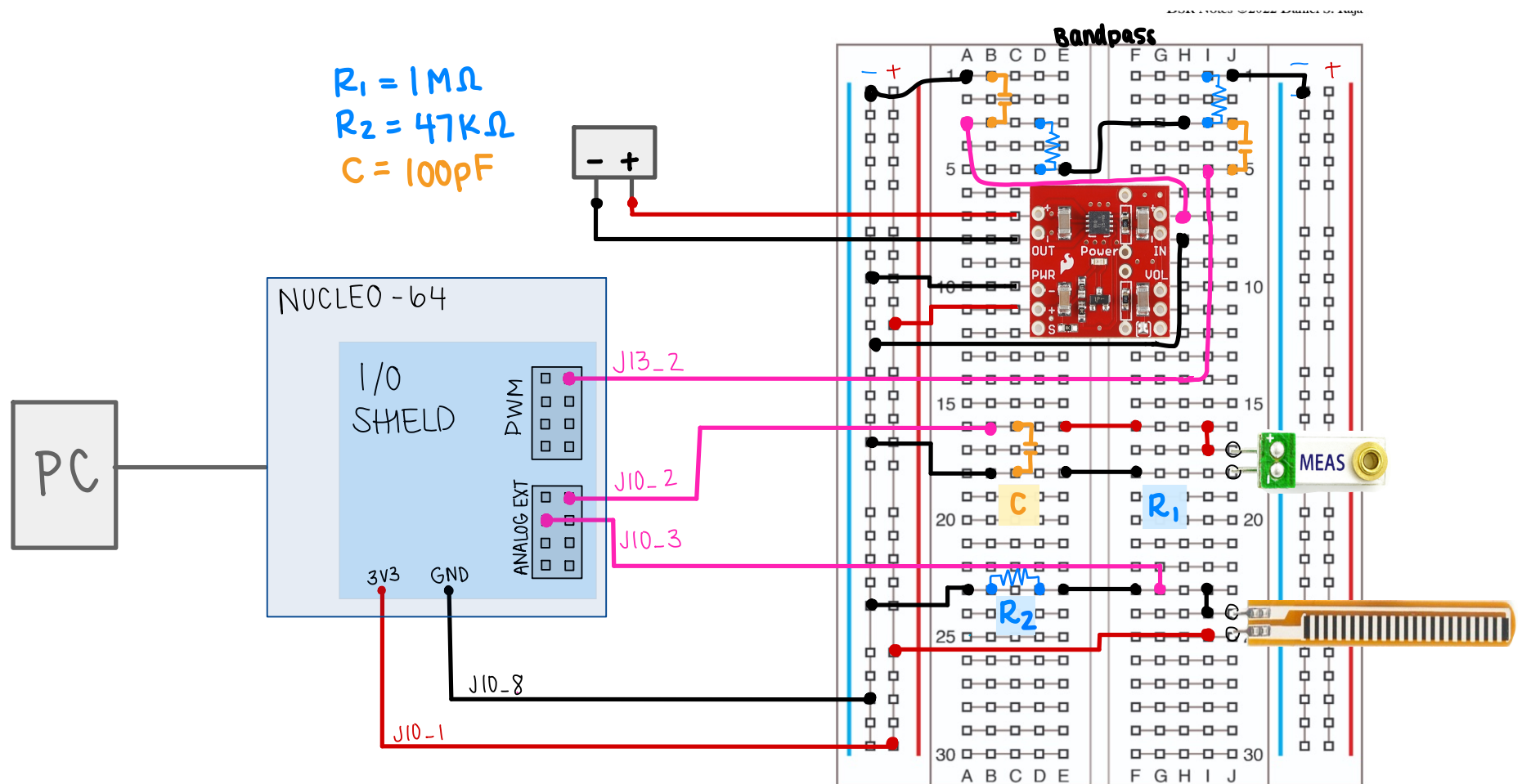


Figure 8: Breadboard Circuit Diagram for NOT Gate Using IC-7400